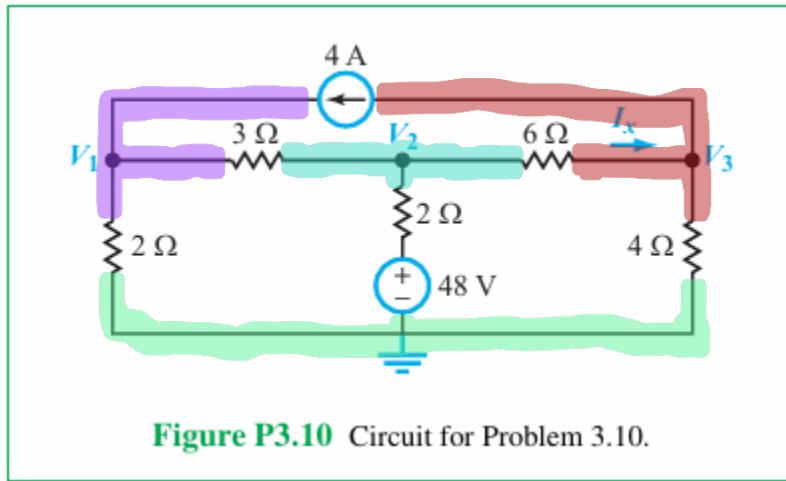


3.10 Apply nodal analysis to find node voltages V_1 to V_3 in the circuit of **Fig. P3.10** and then determine I_x .



$$\text{KCL 1: } \left[\frac{V_1}{2[\Omega]} + \frac{V_1 - V_2}{3[\Omega]} - 4[A] \right] = 0 \cdot 6[\Omega]$$

$$\Rightarrow 3V_1 + 2V_1 - 2V_2 - 24[V] = 0$$

$$= 5V_1 - 2V_2 = 24[V]$$

$$\text{KCL 2: } \left[\frac{V_2 - V_1}{3[\Omega]} + \frac{V_2 - 48[V]}{2[\Omega]} + \frac{V_2 - V_3}{6[\Omega]} \right] = 0 \cdot 6[\Omega]$$

$$= 2V_2 - 2V_1 + 3V_2 - 144[V] + V_2 - V_3 = 0$$

$$\Rightarrow 6V_2 - 2V_1 - V_3 = 144[V]$$

$$\text{KCL 3: } \left[4[A] + \frac{V_3 - V_2}{6[\Omega]} + \frac{V_3}{4[\Omega]} \right] = 0 \cdot 12[\Omega]$$

$$= 48[V] + 2V_3 - 2V_2 + 3V_3 = 0$$

$$= 5V_3 - 2V_2 = -48 \text{ [v]}$$

$$\begin{bmatrix} 5 & -2 & 0 \\ -2 & 6 & -1 \\ 0 & -2 & 5 \end{bmatrix}$$

Matrix A

$$\begin{bmatrix} V_1 \\ V_2 \\ V_3 \end{bmatrix}$$

$$\begin{bmatrix} +24 \\ 144 \\ -48 \end{bmatrix}$$


Matrix B

$$\begin{bmatrix} 16.8 \\ 30 \\ 2.4 \end{bmatrix} \begin{matrix} \frac{84}{5} V_1 \\ 30 V_2 \\ \frac{12}{5} V_3 \end{matrix}$$

$$V_1 = 16.8 \text{ [v]}, V_2 = 30 \text{ [v]}, V_3 = 2.4 \text{ [v]}$$

$$I_x = \frac{V_2 - V_3}{6 \text{ [}\Omega\text{]}} = \frac{30 - 2.4}{6 \text{ [}\Omega\text{]}} = 4.6 \text{ [A]}$$

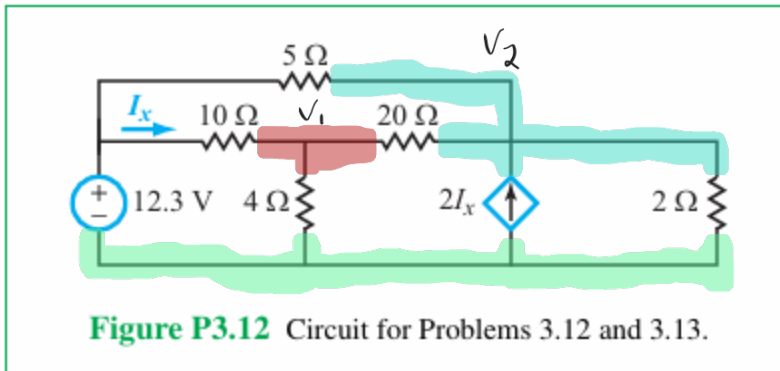3.12 The magnitude of the dependent current source in the circuit of **Fig. P3.12** depends on the current I_x flowing through the $10\ \Omega$ resistor. Determine I_x .



$$KCL1: \left[\frac{V_1 - 12.3 [V]}{10 [\Omega]} + \frac{V_1}{4 [\Omega]} + \frac{V_1 - V_2}{20 [\Omega]} \right] = 0 \quad 20 [\Omega]$$

$$\Rightarrow 2V_1 - 24.6 [V] + 5V_1 + V_1 - V_2 = 0$$

$$= 8V_1 - V_2 = 24.6 [V]$$

$$KCL2: \left[-2I_x + \frac{V_2}{2 [\Omega]} + \frac{V_2 - 12.3}{5 [\Omega]} + \frac{V_2 - V_1}{20 [\Omega]} \right] = 0 \quad 20 \Omega$$

$$-2I_x = -2 \left[\frac{12.3 [V] - V_1}{10} \right] = \left[\frac{V_1 - 12.3}{5} \right] 20 = 4V_1 - 49.2$$

$$= 4V_1 - 49.2 [V] + 10V_2 + 4V_2 - 49.2 + V_2 - V_1 = 0$$

$$\Rightarrow 15V_2 + 3V_1 = 98.4$$


$$\begin{bmatrix} 8 & -1 \\ 1 & 5 \end{bmatrix} \begin{bmatrix} 24.6 \\ 32.8 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$

MatA MatB

$$\begin{matrix} 3.8 \text{ [V]} \\ \Rightarrow 5.8 \text{ [V]} \end{matrix}$$

$$I_x = \frac{12.3 \text{ [V]} - 3.8 \text{ [V]}}{10 \text{ [}\Omega\text{]}} = 0.85 \text{ [A]}$$

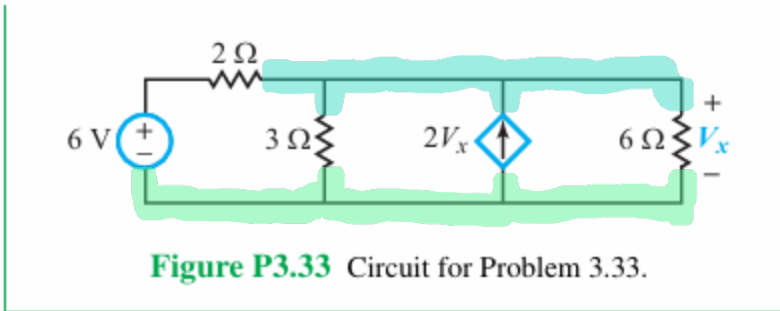3.33 Apply mesh analysis to the circuit in **Fig. P3.33** to determine V_x .




$$\text{KCL: } \left[\frac{V_1 - 6[\text{V}]}{2[\Omega]} + \frac{V_1}{3[\Omega]} - 2V_x + \frac{V_1}{6[\Omega]} \right] = 0 \quad 6[\Omega]$$

$$\Rightarrow 3V_1 - 18[\text{V}] + 2V_1 - 12V_1 + V_1 = 0$$

$$\Rightarrow 6V_1 - 12V_1 = 18[\text{V}]$$

$$\Rightarrow -6V_1 = 18[\text{V}] = -V_1 = 3[\text{V}] \Rightarrow V_1 = -3[\text{V}]$$

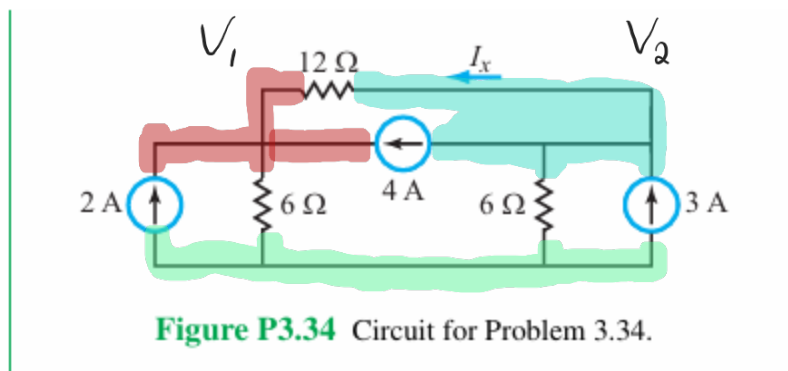3.34 Use the supermesh concept to solve for I_x in the circuit of Fig. P3.34.



$$KCL1: \left[-2[A] + \frac{V_1}{6[\Omega]} - 4[A] + \frac{V_1 - V_2}{12[\Omega]} \right] = 0 \cdot 12\Omega$$

$$= -24[V] + 2V_1 - 48[V] + V_1 - V_2 = 0$$

$$\Rightarrow 3V_1 - V_2 = 72[V]$$

$$KCL2: \left[-3[A] + 4[A] + \frac{V_2}{6[\Omega]} + \frac{V_2 - V_1}{12[\Omega]} \right] = 0 \cdot 12[\Omega]$$

$$= -36[V] + 48[V] + 2V_2 + V_2 - V_1 = 0$$

$$\Rightarrow 3V_2 - V_1 = -12[V]$$

$$\begin{bmatrix} 3 & -1 \\ -1 & 3 \end{bmatrix} \begin{bmatrix} 72 \\ -12 \end{bmatrix} = \begin{bmatrix} 25.5 \\ 4.5 \end{bmatrix} \begin{matrix} V_1 \\ V_2 \end{matrix}$$

MatA

MatB

$$I_x = \frac{V_2 - V_1}{12\Omega} = \frac{4.5 - 25.5}{12}$$

$$= -1.75[A]$$

Repeated Problem, Already Solved

3.37 The circuit in **Fig. P3.37** includes a dependent current source. Apply mesh analysis to determine I_x .

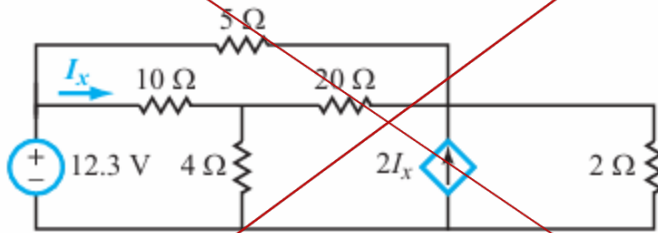


Figure P3.37 Circuit for Problems 3.37 and 3.38.

3.71 Find the Thévenin equivalent circuit at terminals (a,b) of the circuit in **Fig. P3.71**.

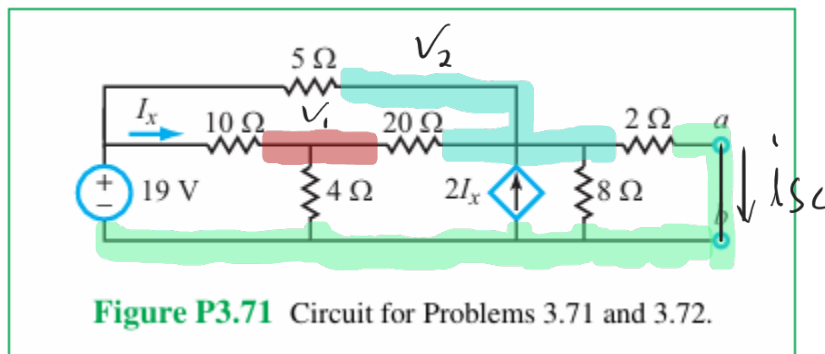


Figure P3.71 Circuit for Problems 3.71 and 3.72.

$$KCL: \left[\frac{V_1 - 19[V]}{10[\Omega]} + \frac{V_1}{4[\Omega]} + \frac{V_1 - V_2}{20[\Omega]} \right] = 0 \quad 20\mu$$

$$= 2V_1 - 38[V] + 5V_1 + V_1 - V_2 = 0$$

$$= 8V_1 - V_2 = 38[V]$$

$$KCL 2: \left[\frac{V_2 - V_1}{20[\Omega]} - 2I_x + \frac{V_2}{8[\Omega]} + \frac{V_2 - 19[V]}{5[\Omega]} \right] = 0 \quad 40\mu$$

$$= 2V_2 - 2V_1 - 40I_x + 5V_2 + 8V_2 - 152[V] = 0$$

$$\Rightarrow 15V_2 - 2V_1 - 40I_x = 152[V]$$

$$I_x = \frac{19 - V_1}{10} \quad \cdot -40 = [4V_1 - 76[V]] \cdot 2 = 8V_1 - 152$$

$$\Rightarrow 15V_2 + 6V_1 = 304[V]$$

$$\begin{bmatrix} 8 & -1 \\ 6 & 15 \end{bmatrix} \begin{bmatrix} 38 \\ 304 \end{bmatrix} = \begin{bmatrix} 6.937 \\ 17.492 \end{bmatrix} \begin{matrix} V_1 \\ V_2 \end{matrix}$$

Mat A Mat B

$$V_{ab} = V_2 = 17.492 [V]$$


KCL For i_{sc} : ~~*~~ $\searrow$ set all $\frac{V_2}{2\Omega}$ to KCL 2:

$$\left[\frac{V_2}{2\Omega} \right] \cdot 40\Omega = 20V_2$$

$$\begin{bmatrix} 8 & -1 \\ 6 & 35 \end{bmatrix} \begin{bmatrix} 38 \\ 304 \end{bmatrix} = \begin{bmatrix} 5.713 \\ 7.406 \end{bmatrix} \begin{matrix} V_1 \\ V_2 \end{matrix}$$

$$i_{sc} = \frac{7.406 [V]}{2 [\Omega]} = 3.853 [A]$$
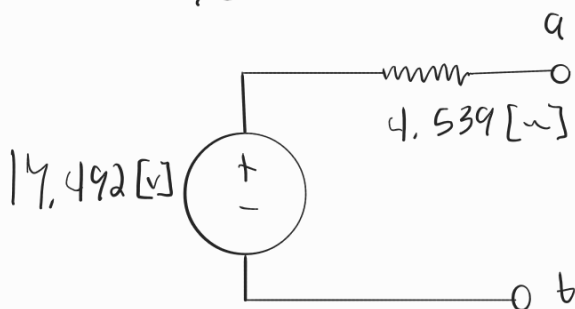
$$R_{Th} = \frac{17.492 [V]}{3.853 [A]} = 4.539 [\Omega]$$



*3.74 Find the Norton equivalent circuit at terminals (a,b) of the circuit in Fig. P3.74.

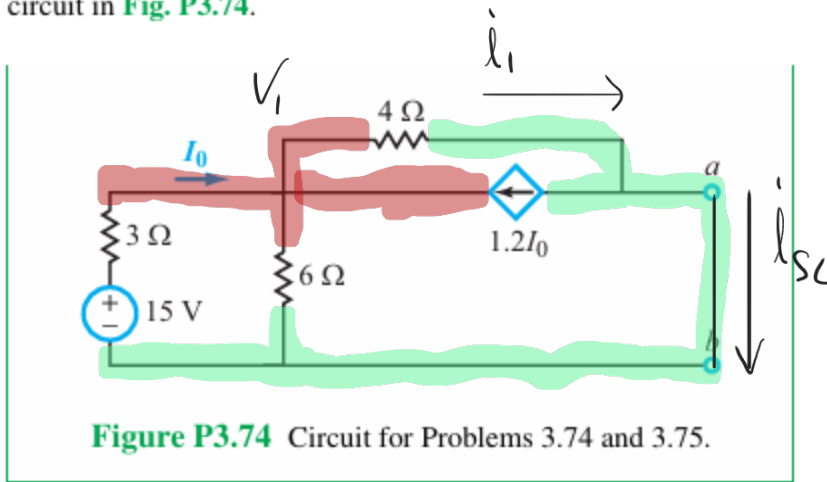


Figure P3.74 Circuit for Problems 3.74 and 3.75.

$$\text{KCL 1: } \left[\frac{V_1 - 15 [\text{V}]}{3 [\Omega]} + \frac{V_1}{6 [\Omega]} + \frac{V_1}{4 [\Omega]} - 1.2 I_0 \right] = 0 \quad | \quad 2 [\sim]$$

$$\Rightarrow 4V_1 - 60 [\text{V}] + 2V_1 + 3V_1 - 14.4 I_0 = 0$$

$$\Rightarrow 9V_1 - 60 [\text{V}] - 14.4 I_0 = 0$$


$$I_0 = \left[\frac{15 [\text{V}] - V_1}{3 [\Omega]} \right] \cdot 14.4 = 72 [\text{V}] - 4.8 V_1$$

$$\Rightarrow 13.8 V_1 - 132 [\text{V}] = 0 \Rightarrow V_1 = \frac{132 [\text{V}]}{13.8} = 9.565 [\text{V}]$$

$$i_1 = \frac{9.565 [\text{V}]}{4 [\Omega]} = 2.391 [\text{A}] \quad i_0 = \frac{15 - 9.565}{3} = 1.811 [\text{A}] \cdot 1.2 = 2.174 [\text{A}]$$

$$i_{sc} = i_1 - 1.2 i_0 = (2.391 - 2.174) [\text{A}] = 217 [\text{mA}]$$

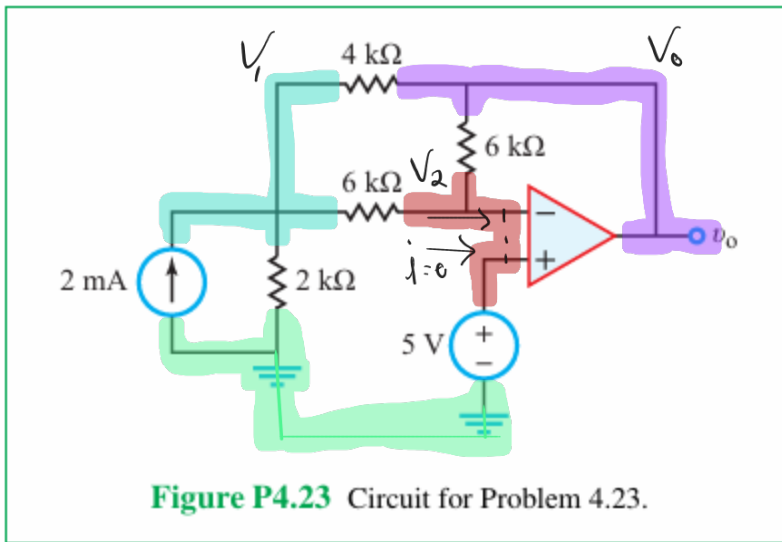*4.23 Find the value of v_o in the circuit in Fig. P4.23.



$$KCL V_2: \left[\frac{V_2 - V_1}{6 \text{ k}\Omega} + \frac{V_2 - V_o}{6 \text{ k}\Omega} \right] = 0 \quad [k\Omega]$$

$$= 2V_2 - V_1 - V_o = 0, V_2 = 5 \text{ [V]} = 10 \text{ [V]} - V_1 - V_o = 0$$

$$\Rightarrow V_o = 10 \text{ [V]} - V_1$$

$$KCL V_1: \left[-2 \text{ [mA]} + \frac{V_1}{2 \text{ k}\Omega} + \frac{V_1 - V_2}{6 \text{ k}\Omega} + \frac{V_1 - V_o}{4 \text{ k}\Omega} \right] = 0 \quad [k\Omega]$$

$$= -24 \text{ [V]} + 6V_1 + 2V_1 - 2V_2 + 3V_1 - 3V_o = 0$$

$$= 11V_1 - 2V_2 - 3V_o - 24 \text{ [V]} = 0 \quad \text{Plug in } V_2 = 5 \text{ [V]}, V_o = 10 \text{ [V]} - V_1$$


$$11V_1 - 3V_o - 24 \text{ [V]} - 3[10 \text{ [V]} - V_1] - 2(5 \text{ [V]})$$

$$\Rightarrow 14V_1 - 64 \text{ [V]} = 0 \text{ [V]}, V_1 = \frac{64 \text{ [V]}}{14} = 4.571 \text{ [V]}$$

$$V_o = 10 [v] - V_i \Rightarrow 10 [v] - 4.571 [v] = 5.429 [v]$$

$$V_o = 5.429 [v]$$

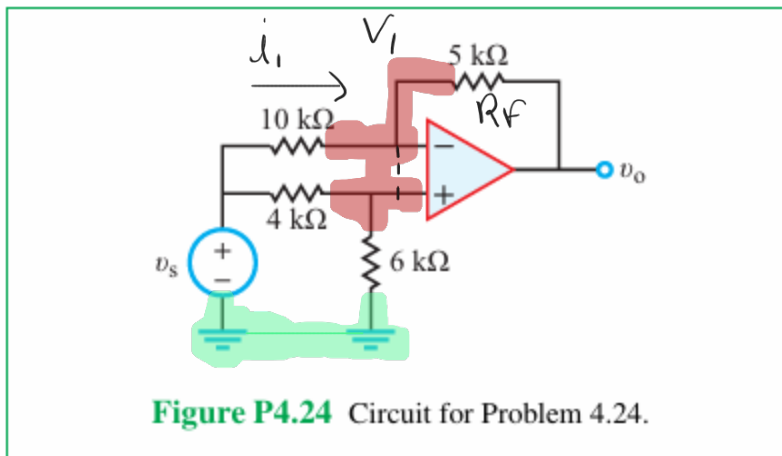4.24 For the circuit in **Fig. P4.24**, obtain an expression for voltage gain $G = v_o/v_s$.



$$V_1 = V_s \left(\frac{6 \text{ k}\Omega}{(6+4) \text{ k}\Omega} \right) \Rightarrow V_1 = 0.6 V_s$$

$$\text{KCL: } \left[\frac{0.6 V_s - V_s}{10 \text{ k}\Omega} + \frac{0.6 V_s - V_o}{5 \text{ k}\Omega} \right] = 0 \quad [V_s]$$

$$= 0.6 V_s - V_s + 1.2 V_s - 2 V_o = 0$$

$$= 0.8 V_s - 2 V_o = 0 \Rightarrow V_o = 0.4 V_s$$

$$V_{R_f} = V_o - V_1 = 0.4 V_s - 0.6 V_s = -0.2 V_s$$

$$G = \frac{V_o}{V_s} = \frac{0.4 V_s}{V_s} = \boxed{0.4}$$